

选择题 (20):

1. C
2. B
3. A
4. C
5. D
6. C
7. D
8. C
9. B
10. C

填空题 (15%):

1. High high low differential common feedback
2. 5(2 point)
3. Operational amplifier negative won't
4. CDAB

问答题:

1 (5%) $I = \frac{6.2 - 0.7}{1.8} \text{ mA}$

2. (a) A negative feedback(5%)

(b) A negative feedback and the input terminal is in the inverting terminal(5%)

3 (15%) (1)

$$\because R_2 = 6.2\text{k} \ll \beta R_{E1} = 150 \times 1.5\text{k} = 225\text{k}$$

$$\therefore V_{B1} \approx \frac{R_2}{R_1 + R_2} V_{DD} = \frac{6.2}{24 + 6.2} \times 15 \approx 3.08 \text{ V}$$

$$\therefore V_{E1} \approx V_{B1} - 0.7 \approx 3.08 - 0.7 = 2.38 \text{ V}$$

$$\therefore I_{E1} = \frac{V_{E1}}{R_{E1}} = \frac{2.38}{1.5\text{k}} \approx 1.59 \text{ mA}$$

Assume Q_1 works in linear region, then

$$I_{C1} = \frac{\beta}{\beta + 1} I_{E1} \approx 1.58 \text{ mA}$$

$$\therefore V_{C1} = V_{DD} - I_{C1} R_{C1} \approx 15 - 1.58 \times 5.1 \approx 6.94 \text{ V}$$

$$\therefore V_{CE1} = V_{C1} - V_{E1} \approx 6.94 - 2.38 = 4.56 \text{ V} > 0.7 \text{ V}$$

Q_1 working in linear region is checked.

Since two transistors are biased identically, they have same bias voltages and currents.

$$r_{e1} = r_{e2} = \frac{V_T}{I_C} = \frac{26}{1.58} \approx 16.5 \Omega$$



$$(2) A_{v1} \approx -\frac{R_{L1}}{r_{e1}} \approx -\frac{R_{C1} \parallel R_1 \parallel R_2 \parallel \beta r_{e2}}{r_{e1}} \approx -\frac{1245}{16.5} \approx -75.5$$

$$A_{v2} \approx -\frac{R_{L2}}{r_{e2}} \approx -\frac{R_{C2}}{r_{e1}} \approx -\frac{5.1k}{16.5} \approx 309.1$$

$$A_v = A_{v1} A_{v2} \approx 75.5 \times 309.1 \approx 23337 \text{ for no-loading case}$$

$$(3) A'_v = A_{v1} A'_{v2} \approx 75.5 \times \frac{5.1k \parallel 5.1k}{16.5} \approx 11669$$

4. (10%)

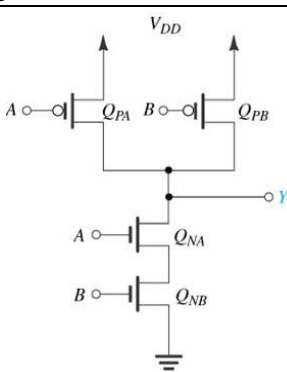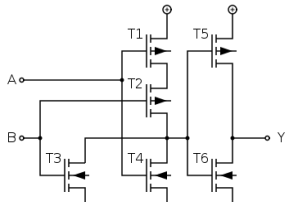Logic circuit	Truth table	Function															
	<p>4%</p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>1</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>0</td></tr> </tbody> </table>	A	B	Y	0	0	1	0	1	1	1	0	1	1	1	0	<p>1%</p> <p>NAND $Y = \overline{A \cdot B}$</p>
A	B	Y															
0	0	1															
0	1	1															
1	0	1															
1	1	0															
	<p>4%</p> <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>1</td></tr> <tr> <td>1</td><td>0</td><td>1</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	1	1	0	1	1	1	1	<p>1%</p> <p>OR $Y = A + B$</p>
A	B	Y															
0	0	0															
0	1	1															
1	0	1															
1	1	1															

5.

$$(1) v_o(t) = -RC \frac{dv_1(t)}{dt} \quad (5\%)$$

$$(2) (15\%) \text{ a \& b. } v_{2-} = V_2; \quad V_{1-} = V_1$$

$$V_{o2} = V_2 + R \frac{V_2 - V_1}{R_p} = 1.1V_2 - 0.1V_1$$

$$V_{o1} = V_1 - R \frac{V_2 - V_1}{R_p} = 1.1V_1 - 0.1V_2$$

$$\text{c. } V_o = V_{o1} - V_{o2}$$

$$\text{d. } V_o = V_{o1} - V_{o2} = (1.1V_1 - 0.1V_2) - (1.1V_2 - 0.1V_1) = 10.5 - 4.5 = 6 \text{ V}$$

6 (5%)

$$I_1 = \frac{V_{REF}}{R_1} = 1 \mu A$$
$$I_2 = \frac{(W/L)_2}{(W/L)_1} I_1 = 0.5 \mu A$$