







# 中山大学理工学院 2013 学年 2 学期 期中 12 级微电子 2+2 模拟电子技术 试卷 (A)

\_\_\_\_ 年级 \_\_\_\_ 专业 姓名 \_\_\_\_\_ 学号 \_\_\_\_\_



老师姓名:

考试成绩 :

1. Assuming all diodes to be ideal, draw the output waveform for each rectifier circuit. (15%)

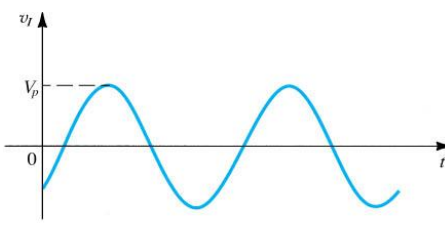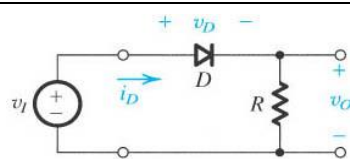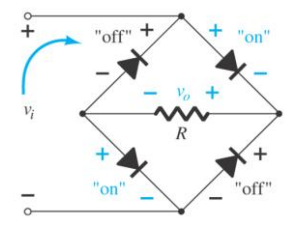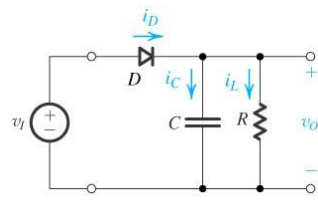Input waveform	Rectifier configurations	Output Waveforms
 <p>(b)</p>	 <p>(a)</p>	
		
	 <p>(a)</p>	

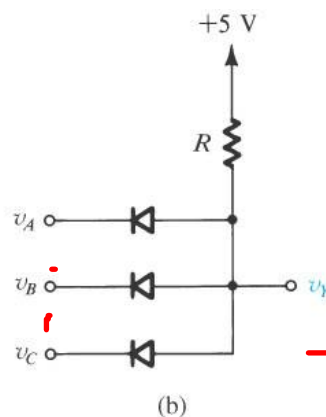
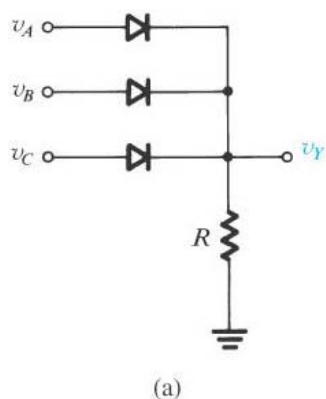
2. Assume all diodes to be ideal. Figure out the types of the below logic gates and write the relevant truth tables (10%)



(a): <u>          </u> gate				(b): <u>          </u> gate			
$v_A$	$v_B$	$v_C$	$v_Y$	$v_A$	$v_B$	$v_C$	$v_Y$
0	0	0	0	0	0	0	0
0	0	1		0	0	1	
0	1	0		0	1	0	
0	1	1		0	1	1	
1	0	0		1	0	0	
1	0	1		1	0	1	
1	1	0		1	1	0	
1	1	1		1	1	1	

Note: logic “1” means high voltage, i.e., around 5V, and logic “0” means low voltage, i.e., around 0V.

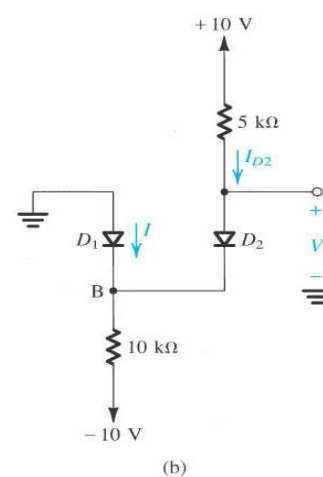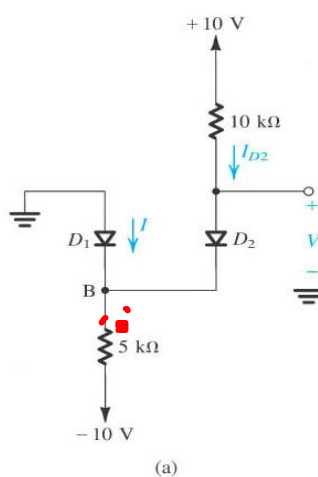3. Assuming the diodes to be ideal, find the values of  $I$  and  $V$  in the following circuits (20%)




4. Fill in the blank areas (30%)


- (1) The single-crystal formed by pure semiconductor materials is called \_\_\_\_\_ semiconductor.
- (2) The materials containing impurity atoms are called \_\_\_\_\_ semiconductors, or doped semiconductors.
- (3) In  $n$ -type semiconductors, the impurities are from group \_\_\_\_ elements, e.g. Phosphorus.
- (4) In  $p$ -type semiconductors, the impurities are from group \_\_\_\_ elements, e.g. Boron.
- (5) The majority carriers in  $n$ -type materials are \_\_\_\_\_.
- (6) The minority carriers in  $n$ -type materials are \_\_\_\_\_.
- (7) When doing DC analysis, the capacitor can be treated as \_\_\_\_\_ circuit and the inductor can be treated as \_\_\_\_\_ circuit. When doing AC analysis, the independent voltage source can be treated as \_\_\_\_\_ circuit. (select open or short)
- (8) The condition of a BJT working in active regions is that the BE junction is \_\_\_\_\_ bias and the BC junction is \_\_\_\_\_ bias. As for BJT working in saturation region, the condition is that the BE junction is \_\_\_\_\_ bias and the BC junction is \_\_\_\_\_ bias. (select forward or reverse)
- (9) For a BJT amplifier with common-emitter configuration, the input terminal is \_\_\_\_\_, and the out terminal is \_\_\_\_\_.

5. (20%) A BJT cascade amplifier is shown below. Assuming  $V_{BE(on)}$  is 0.7 V,

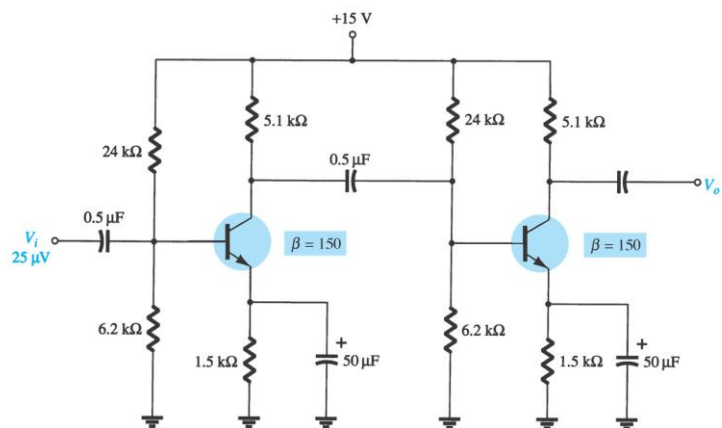- (1) Calculate the dc bias voltages ( $V_B$ ,  $V_C$  and  $V_E$ ) and collector current ( $I_C$ ) of each stage;
- (2) Calculate the input impedance, output impedance and the overall ac voltage gain.



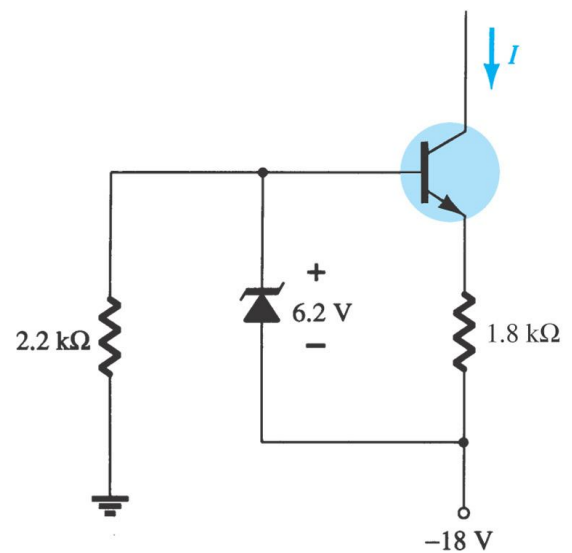6. Assuming  $V_{BE(\text{on})}$  is 0.7 V, calculate the constant current  $I$  in the following circuit. (5%)



The End