










中山大学理工学院 2013 学年 2 学期 期中 12 级微电子 2+2 模拟电子技术 试卷参考答案

____ 年级 ____ 专业 姓名 ____ 学号 ____


老师姓名：

考试成绩：

1. Assuming all diodes to be ideal, draw the output waveform for each rectifier circuit. (15%)

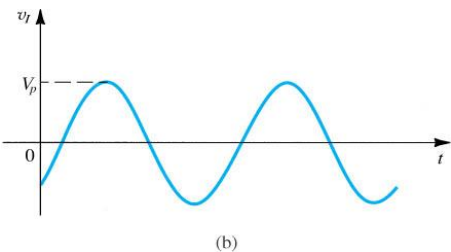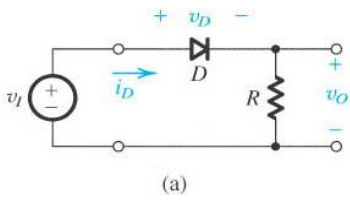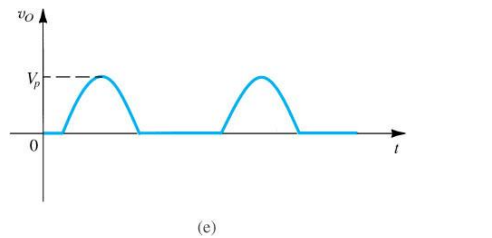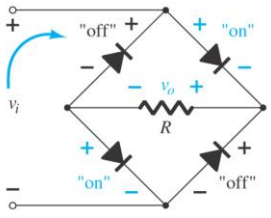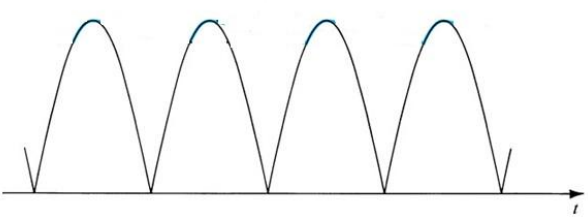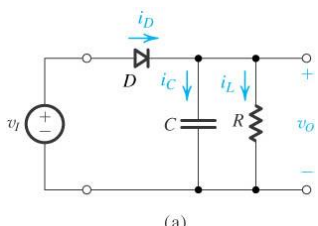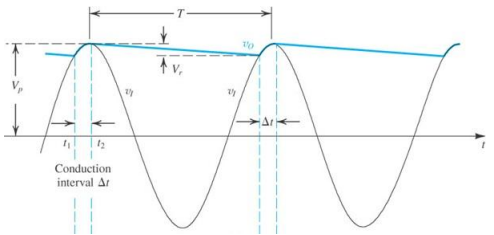Input waveform	Rectifier configurations	Output Waveforms
		
		
		

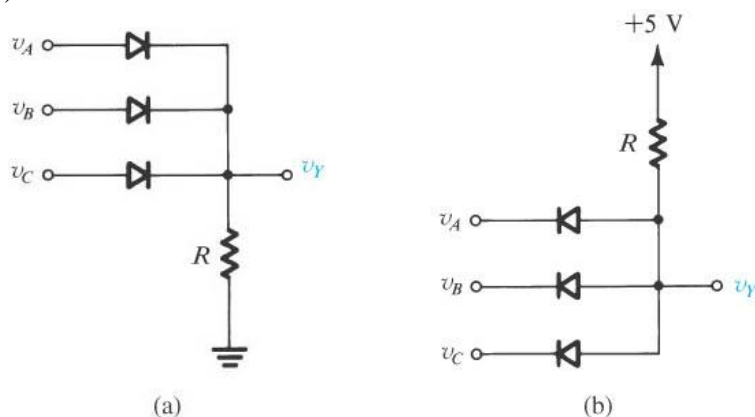
2. Assume all diodes to be ideal. Figure out the types of the below logic gates and write the relevant truth tables (10%)



(a): OR gate				(b): AND gate			
v_A	v_B	v_C	v_Y	v_A	v_B	v_C	v_Y
0	0	0	0	0	0	0	0
0	0	1	1	0	0	1	0
0	1	0	1	0	1	0	0
0	1	1	1	0	1	1	0
1	0	0	1	1	0	0	0
1	0	1	1	1	0	1	0
1	1	0	1	1	1	0	0
1	1	1	1	1	1	1	1

Note: logic “1” means high voltage, i.e., around 5V, and logic “0” means low voltage, i.e., around 0V.

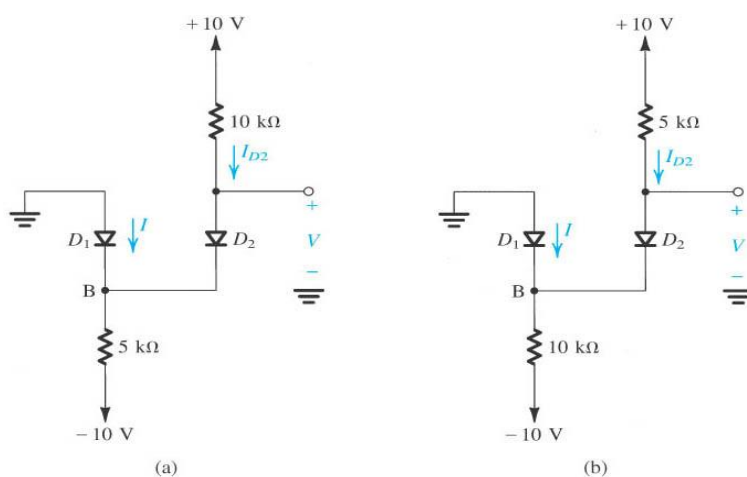3. Assuming the diodes to be ideal, find the values of I and V in the following circuits (20%)



(a) It is easy to decide that D2 is in state ON, or V_B are supposed to be higher than 10Volts, which is impossible. So we have only two assumptions to filter. One is that both D1 and D2 are on, otherwise D2 is on and D1 is off.

For the first assumption, we can get $V_B = 0$ V, So:

$$I_{D2} = \frac{(10-0)V}{10K\Omega} = 1(mA)$$

$$V = V_B = 0(V)$$

$$I_{5K\Omega} = \frac{[V_B - (-10)]V}{5K\Omega} = 2(mA)$$

$$I = I_{5K\Omega} - I_{D2} = 1(mA)$$

This assumption is correct, and the other assumption is wrong surely. The detail steps to prove can be done by you easily as the similar method above.

(b) Compared with (a), the difference is the two resistors changed their positions. Firstly, we can also decide that the D2

is always on as the same reason in (a). Therefore, we also have only two choices.

First, we assume that D1 is on when D2 is on.

If D1 is on, $V_B=0V$. So:

$$I_{10K\Omega} = \frac{[0 - (-10)]V}{10k\Omega} = 1(mA)$$

$$I_{D2} = \frac{10V}{5K\Omega} = 2(mA) \quad \text{Since } I < 0, \text{ it is not consistent with our assumption. The first assumption is not}$$

$$I = I_{10K\Omega} - I_{D2} = -1(mA) < 0$$

correct, which mean the second assumption must be right.


Second, we can get that D1 in off when D2 is on. So $I=0$.

$$V = 10 - \frac{[10 - (-10)]V}{15K\Omega} \times 5K\Omega = \frac{10}{3}V \approx 3.3V.$$


4. Fill in the blank areas (30%)

- (1) The single-crystal formed by pure semiconductor materials is called intrinsic semiconductor.
- (2) The materials containing impurity atoms are called extrinsic semiconductors, or doped semiconductors.
- (3) In *n*-type semiconductors, the impurities are from group V elements, e.g. Phosphorus.
- (4) In *p*-type semiconductors, the impurities are from group III elements, e.g. Boron.
- (5) The majority carriers in *n*-type materials are electrons.
- (6) The minority carriers in *n*-type materials are holes.
- (7) When doing DC analysis, the capacitor can be treated as open circuit and the inductor can be treated as short circuit. When doing AC analysis, the independent voltage source can be treated as short circuit. (select open or short)
- (8) The condition of a BJT working in active regions is that the BE junction is forward bias and the BC junction is reverse bias. As for BJT working in saturation region, the condition is that the BE junction is forward bias and the BC junction is forward bias. (select forward or reverse)
- (9) For a BJT amplifier with common-emitter configuration, the input terminal is base, and the out terminal is collector.

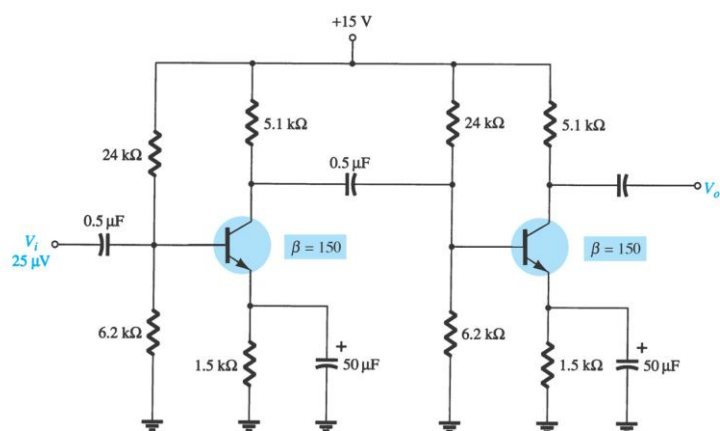5. (20%) A BJT cascade amplifier is shown below. Assuming $V_{BE(on)}$ is 0.7 V,
- (1) Calculate the dc bias voltages (V_B , V_C and V_E) and collector current (I_C) of each stage
 - (2) Calculate the input impedance, output impedance and the overall ac voltage gain.



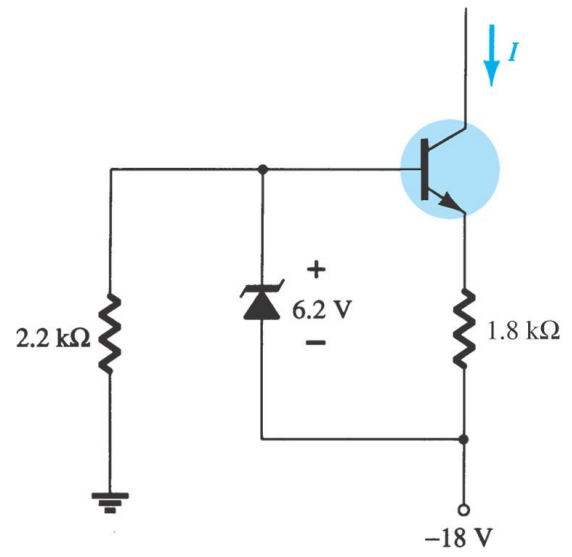6. Assuming $V_{BE(on)}$ is 0.7 V, calculate the constant current I in the following circuit. (5%)



The End