







# 中山大学理工学院 2012 学年 1 学期期末 11 级微电子 2+2 模拟电子技术 试卷 (A)

\_\_\_\_\_ 年级 \_\_\_\_\_ 专业 姓名 \_\_\_\_\_ 学号 \_\_\_\_\_




老师姓名:

考试成绩 :


1. Assuming all diodes are ideal, draw the output waveform for each rectifier circuit. (10%)

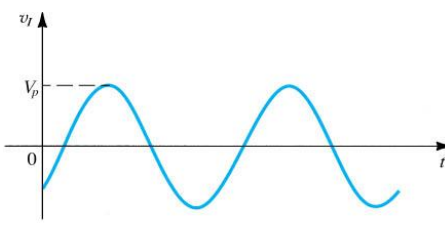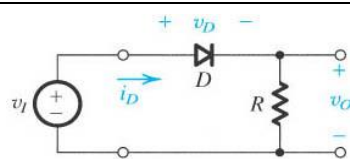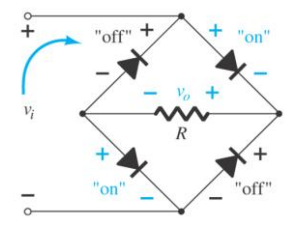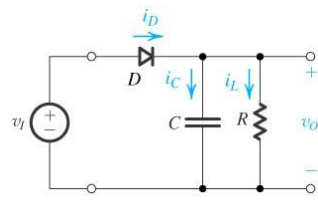Input waveform	Rectifier configurations	Output Waveforms
 <p style="text-align: center;">(b)</p>	 <p style="text-align: center;">(a)</p>	
		
	 <p style="text-align: center;">(a)</p>	


2. Fill in the blank areas (10%)

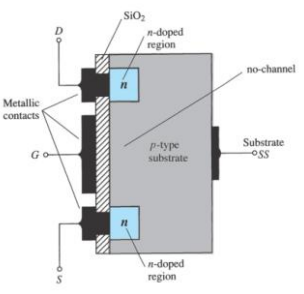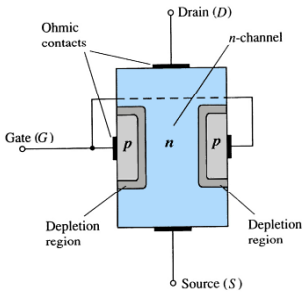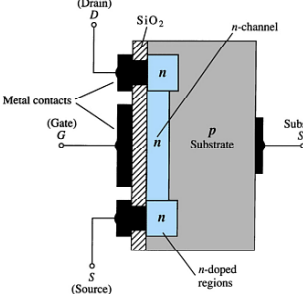FET Structure			
FET Type			
Operation Mode (Tick your selection)	Depletion (D)    ( ) Enhancement (E)    ( )	Depletion (D)    ( ) Enhancement (E)    ( )	Depletion (D)    ( ) Enhancement (E)    ( )
Difference between D- and E- operations			

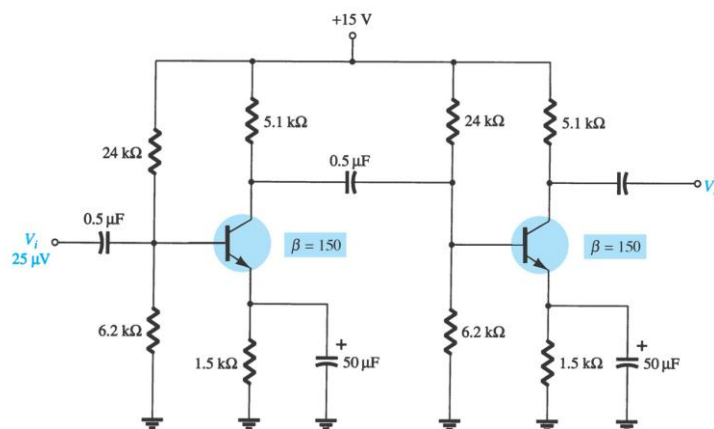3. (15%) A BJT cascade amplifier is shown below. Assuming  $V_{BE(on)}$  is 0.7 V,
1. Calculate the dc bias voltages, collector current and voltage gain of each stage
  2. Calculate the overall ac voltage gain.



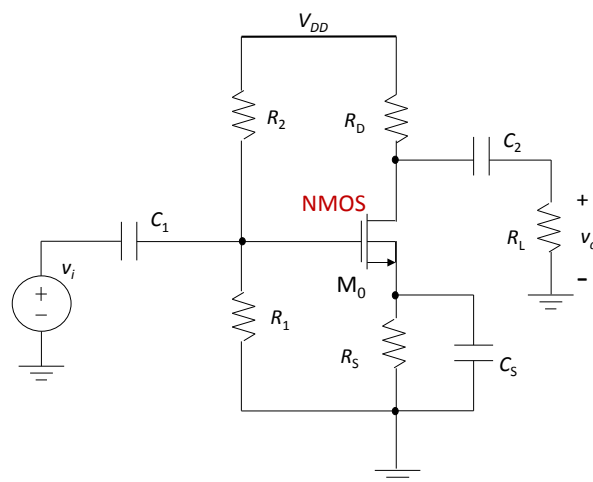4. A single-stage amplifier with N-type enhancement MOSFET is shown below. (10%)
- (1) Draw the DC equivalent circuit.
  - (2) List the equations to decide  $I_D$  and  $V_{DS}$  of NMOSFET  $M_0$  if I-V relationship of  $M_0$  is given as  $I_{D0} = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (V_{GS} - V_{TH})^2 (1 + \lambda V_{DS})$ . Ignore channel length modulation effect in this step.
  - (3) Draw the AC equivalent circuit based on small-signal modeling of  $M_0$ . Write the expression of overall voltage gain ( $v_o/v_i$ ). Channel length modulation effect should be included in this step.




5. Fill in the blank areas (10%)



Logic circuit	Truth table	Function															
	4% <table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td></td></tr> <tr> <td>0</td><td>1</td><td></td></tr> <tr> <td>1</td><td>0</td><td></td></tr> <tr> <td>1</td><td>1</td><td></td></tr> </tbody> </table>	A	B	Y	0	0		0	1		1	0		1	1		1%
A	B	Y															
0	0																
0	1																
1	0																
1	1																
4%	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>Y</th></tr> </thead> <tbody> <tr> <td>0</td><td>0</td><td>0</td></tr> <tr> <td>0</td><td>1</td><td>0</td></tr> <tr> <td>1</td><td>0</td><td>0</td></tr> <tr> <td>1</td><td>1</td><td>1</td></tr> </tbody> </table>	A	B	Y	0	0	0	0	1	0	1	0	0	1	1	1	1%
A	B	Y															
0	0	0															
0	1	0															
1	0	0															
1	1	1															

## 6. Comparator circuits analysis (10%)

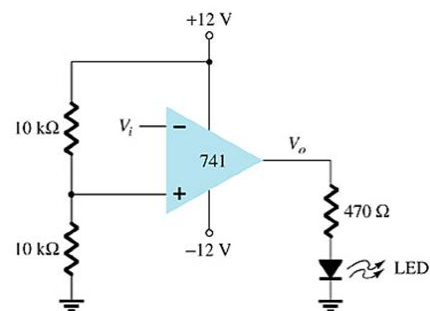(1) Explain the function of the circuit shown below. What will be happened if  $V_i$  is very noisy?




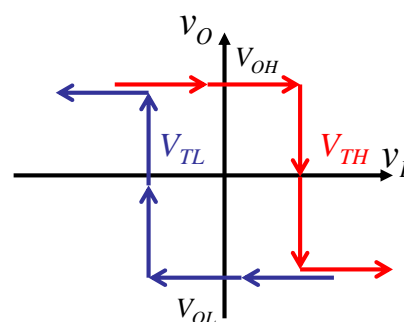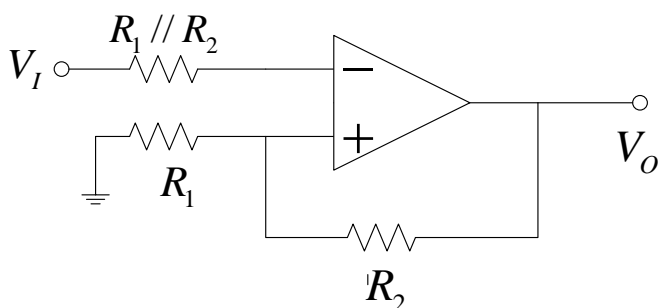(2) Explain the function of Schmitt Trigger shown below. Why the hysteresis operation is introduced in this configuration?




## 7. Op-Amp application circuits (20%)

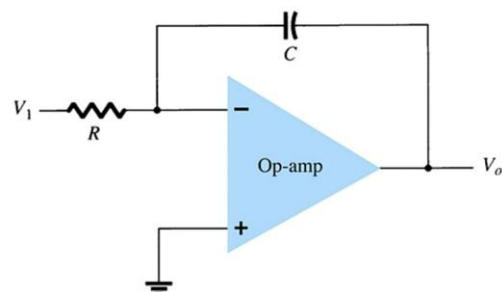(1) Find the relationship between  $V_i$  and  $V_o$  (5%)



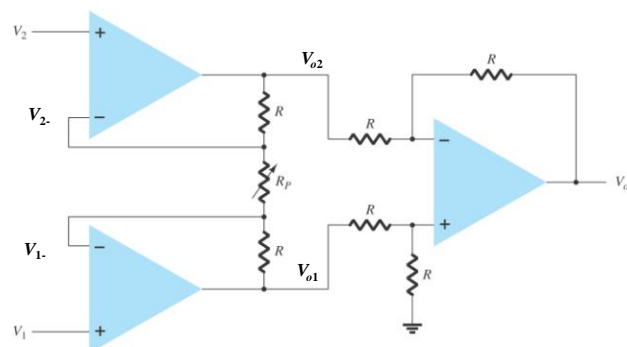(2) For the instrumentation amplifier circuit shown below,  $R = 5 \text{ k}\Omega$ ,  $R_P = 500 \Omega$ , and all operational amplifiers are ideal. (15%)

- Find the relationship between  $V_1, V_2$  and  $V_{o2}$
- Find the relationship between  $V_1, V_2$  and  $V_{o1}$
- Find the relationship between  $V_{o1}, V_{o2}$  and  $V_o$
- Find the value of  $V_o$  if  $V_2 = 10 \text{ V}$  and  $V_1 = 5 \text{ V}$




## 8. Feedback types and feedback circuit analysis (15%)

(1) Fill in the blank areas

Feedback configurations		
Feedback type		
Close-loop gain		
Close-loop $R_{in}$		
Close-loop $R_{out}$		

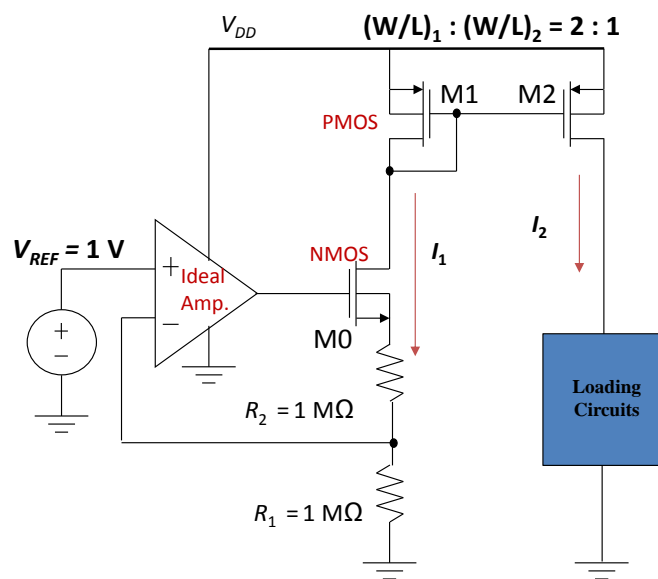(2) A CMOS circuit with negative feedback configuration is shown below. Assuming the amplifier is ideal and all enhancement MOSFETs are working in saturation mode.

- Find the values of  $I_1$  and  $I_2$
- Comments on the circuit function
- What is the feedback type?



The End